

4.) Určete A_u , A_i ;

$$R_L \ll R_3 \quad \left[A'_2 = \frac{R_L}{h_{11}} h_{21} \right]$$

$$I_b = \frac{U_1}{h_{11}} \quad U_2 = (R_3 \parallel R_L) \cdot h_{21} \cdot I_b \Rightarrow \frac{U_2}{U_1} = \frac{(R_3 \parallel R_L)}{h_{11}} \cdot h_{21} = A_u$$

$$\frac{I_b}{I_1} = \frac{\frac{1}{h_{11}}}{\frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{h_{11}}} = \frac{0,256 \text{ mS}}{0,0408 + 0,011 + 0,256} = D = 0,847$$

$$\frac{I_2}{I_c} = \frac{\frac{1}{R_L}}{\frac{1}{R_L} + \frac{1}{R_3}} = 1 \Rightarrow I_2 = \frac{R_3}{R_L + R_3} \cdot h_{21} \cdot I_b = \frac{R_3}{R_L + R_3} h_{21} \cdot D \cdot I_1$$

Preciz?

$$A_i = \frac{R_3}{R_L + R_3} D \cdot h_{21} \approx h_{21}$$

$$R_L \ll R_3$$

$$h_{11} \ll R_2$$

5.)

Vstupní odpor

$$R_{vst} = R_1 \parallel R_2 \parallel h_{11} \approx h_{11}$$

Výstupní odpor

$$R_{vyt} = R_3 \parallel \frac{1}{h_{22}} \approx R_3$$